



北京大学
PEKING UNIVERSITY

智能硬件体系结构

第二讲：电路基础-晶体管与数字电路设计

主讲：陶耀宇、李萌

2024年秋季

- 培养学生初步理解**智能时代的硬件芯片的工作原理、设计原理与未来发展方向**

课程名称	智能硬件体系结构 Hardware Architecture for Intelligent computing Systems
课程编号	04632042
学分	2 学分
总学时	34 学时
上课时间	1-16周 每周周三 5-6节
上课地点	一教 202
考核方式	- 作业 8 次：20%， (2 周 1次, 1 次 3-5 题) - 2次编程实验：2*20%， (传统体系结构、简单 AI 加速器) - 期末考试：30% - 出勤：10%
授课教师	陶耀宇，李萌

注意事项

- 课程作业情况

第1次作业题将在**9.20日周五**放在课程网站上

作业提交截止日期是国庆节后的**10月8日**

作业内容将涵盖9.18和9.25号的课程内容

第1次编程作业：**10月8号~11月8号**

- FSM状态机电路设计
- 存储器电路 – SRAM/DRAM/Flash
- 量化的概念
- Verilog语言基础
- 芯片物理设计基础

2024年秋季学期

主讲：陶耀宇、李萌

目 录




CONTENTS



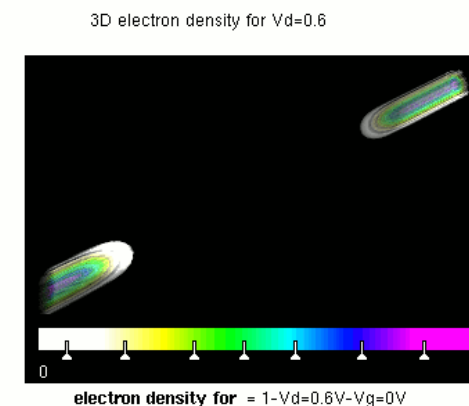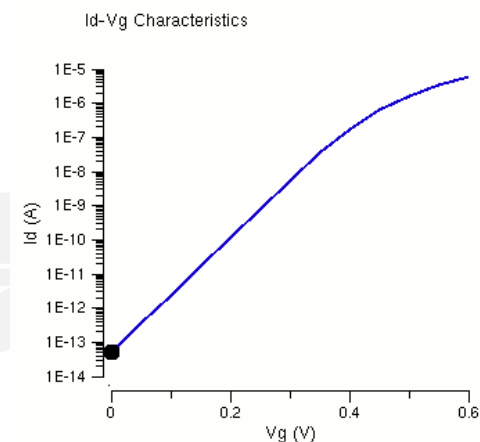 - 01. CMOS晶体管与静态逻辑**
- 02. 电路延迟分析与逻辑功效**
- 03. 动态逻辑电路与时序电路**
- 04. 复杂计算单元与线路分析**


MOSFET晶体 – 现代芯片的基石

- MOSFET有三个工作区间：断开、线性（欧姆区间）、饱和（电压不随电流线性增加）



MOSFET晶体 – 现代芯片的基石

• NMOS与PMOS

 


NMOS

When the **gate is at a low voltage**:

- § P-type body is at low voltage
- § Source-body and drain-body diodes are OFF
- § No current flows, transistor is OFF

• NMOS与PMOS

 


NMOS

When the **gate is at a high voltage**:

- § Positive charge on gate of MOS capacitor; Negative charge attracted to body
- § Inverts a channel under gate to n-type
- § Now current flow through n-type silicon through channel, transistor ON

MOSFET晶体 – 现代芯片的基石

• NMOS与PMOS

 


Similar, but doping and voltages reversed


- § Body tied to high voltage (VDD)
- § Gate low: transistor ON
- § Gate high: transistor OFF

MOSFET作为开关的行为级模型

- NMOS、PMOS和简单反相器


 


NMOS






 


PMOS

$g = 0$

 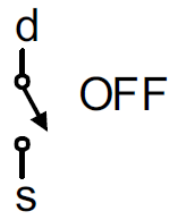

$g = 1$

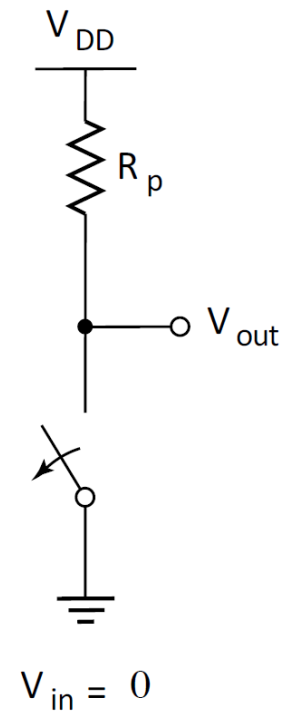     


- NMOS、PMOS可以组成PDN和PUN

- 经典静态逻辑电路

- Differential Cascode Voltage Switch (DCVS)
- Pass Gate Logic (传输门逻辑电路)

主讲：陶耀宇、李萌

- NMOS、PMOS可以组成PDN和PUN

 


PUN and PDN are *dual* networks

- 由PDN和PUN组成的NAND门电路

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

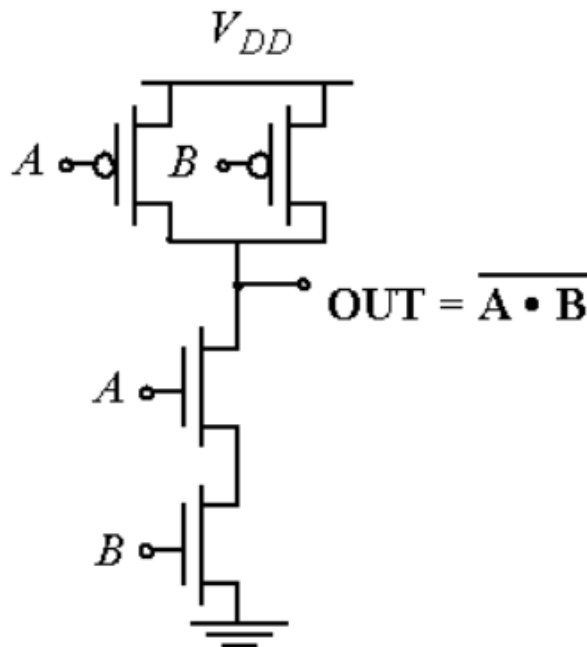

PDN: Connects OUT to ground when $A \cdot B = 1$

PUN: Connects OUT to V_{dd} when $\overline{A} + \overline{B} = 1$

So $OUT =$ Complement of PDN function

Also $OUT =$ PUN function with each input inverted

- 由PDN和PUN组成的复杂静态逻辑电路

$$F = \overline{D + (A(B + C))}$$



Create PDN directly, ignoring inversion

Ex: $D + X$ means that D should be in parallel with X

Identify subnets of PDN

Inside SN3, B and C are parallel, so in PUN, they will be series


Continue in bottom up fashion

  

作业题

• 简单1bit加法器电路

■ $A[n-1:0] + B[n-1:0] = S[n-1:0]$

 


A	B	C_{in}	C_{out}	S	carry status
0	0	0	0	0	kill
0	0	1	0	1	kill
0	1	0	0	1	propagate
0	1	1	1	0	propagate
1	0	0	0	1	propagate
1	0	1	1	0	propagate
1	1	0	1	0	generate
1	1	1	1	1	generate

- $C_o = AB + BC_i + AC_i = AB + (A + B)C_i$
- $S = A \oplus B \oplus C_i = ABC_i + \overline{C_o}(A + B + C_i)$
- $G = AB, K = \overline{A}\overline{B}, P = A \oplus B$

• 简单1bit加法器电路

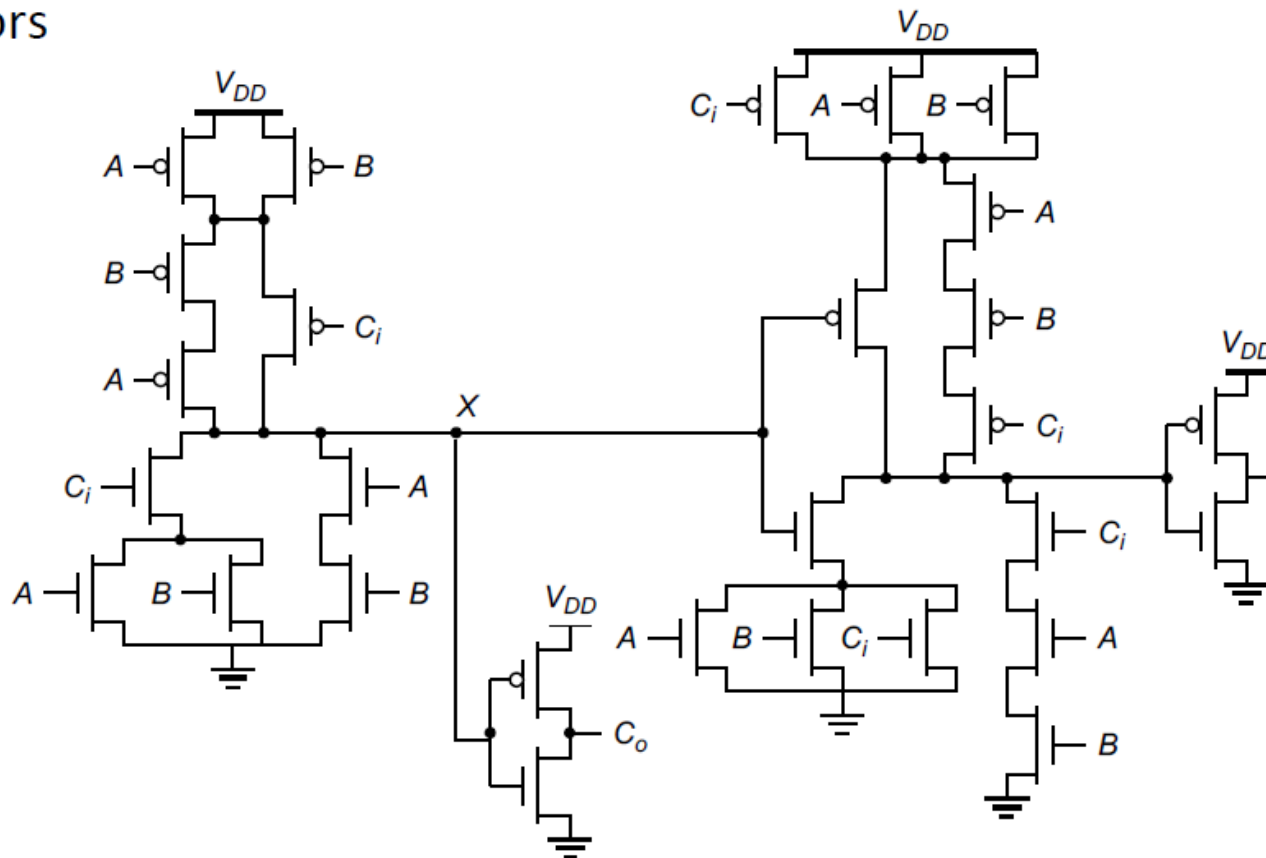- $C_o = AB + BC_i + AC_i = AB + (A + B)C_i$
- $S = A \oplus B \oplus C_i = ABC_i + \overline{C_o}(A + B + C_i)$
- 28 transistors




- NMOS、PMOS可以组成PDN和PUN

- 经典静态逻辑电路
 - Differential Cascode Voltage Switch (DCVS)
 - Pass Gate Logic (传输门逻辑电路)

主讲：陶耀宇、李萌


DCVS静态逻辑电路

• 简单的AND/NAND电路

 

作业题

- 简单的AND/NAND电路

 

- Advantages:

- No PMOS duality
 - Lower input cap.
 - Use only NMOS
- Faster than CMOS
- Can evaluate complex logic trees in 1 stage

- Disadvantages:




- Need complementary inputs (dual rail)
 - Sensitive to input timing
- Cross-bar current
 - Too large → PDN does not switch the output
 - Too small → Slow rise time

- NMOS、PMOS可以组成PDN和PUN

- 经典静态逻辑电路
 - Differential Cascode Voltage Switch (DCVS)
 - Pass Gate Logic (传输门逻辑电路)

主讲：陶耀宇、李萌

• 传输门型电路 – Pass Transmission Logic

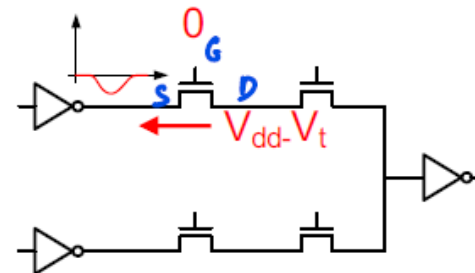  


- Advantages:
 - Speed: 20-50% faster (less capacitance)
 - In some circuits, such as XOR/MUX
 - Lower dynamic power

- Disadvantages:
 - Very sensitive to noise: 2 types
 - V_t drop $\rightarrow$ must level restore someplace
 - Sensitive to undershot voltage noise on inputs
 - Buffers at inputs suppresses this effect
 - Body effect $\rightarrow$ limit # of FETs in series

- 传输门型电路 – Pass Transmission Logic

A	B	Q
1	1	1
0	1	0
1	0	0
0	0	1

xnor

 

Dual rail pass gate logic with differential cascode voltage switch logic

- Combination of DCVS and PTL, Very fast
- Strong PMOS, slow fall; Weak PMOS, slow rise

目 录




CONTENTS



- 01. CMOS晶体管与静态逻辑**
- 02. 电路延迟分析与逻辑功效**
- 03. 动态逻辑电路与时序电路**
- 04. 复杂计算单元与线路分析**

什么是电路的延迟


- 以Inverter反相器为例

   

什么是电路的延迟

- 一阶RC延迟分析

A First-Order RC Network

 


$$V_{out}(t) = (1 - e^{-t/\tau}) V_{DD} = \frac{1}{2} V_{DD}$$

$$\tau = R \times C$$

$$t_p = \ln(2)\tau = 0.69R \times C \quad t = \ln(2)\tau$$


反相器延迟

- 利用一阶RC延迟分析方法

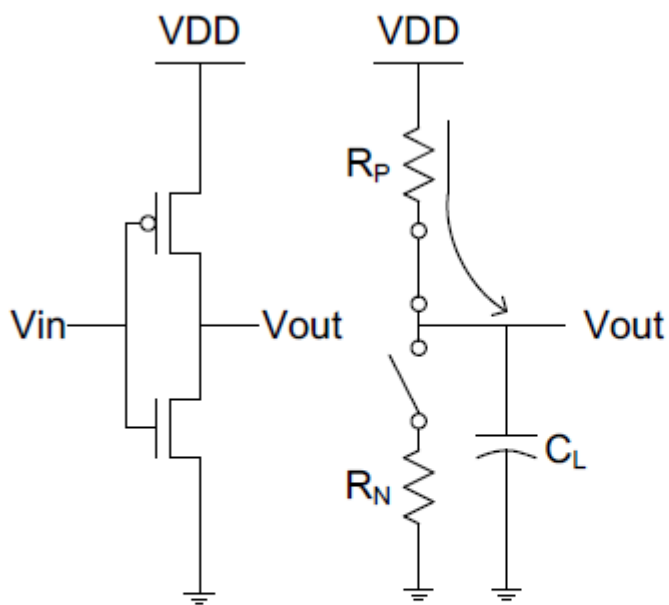

$$V_{in} = 0$$

(a) Low-to-high

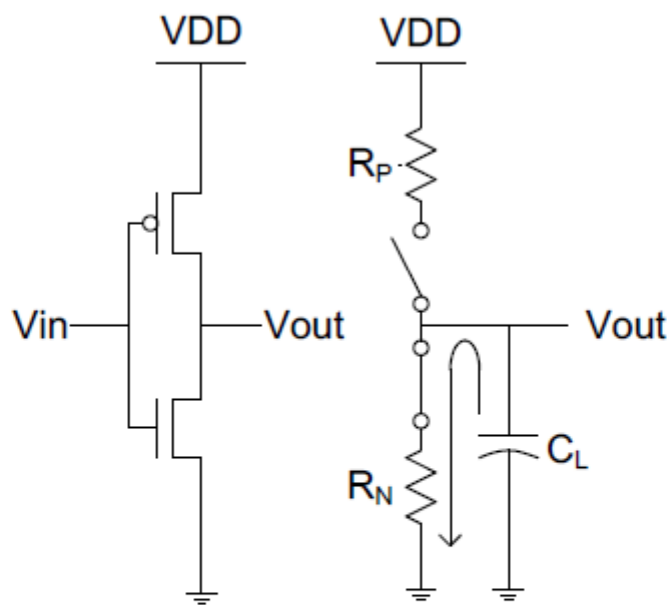

$$V_{in} = V_{DD}$$

(b) High-to-low

$$t_{pHL} = f(R_N \times C_L)$$

$$t_{pHL} = 0.69 R_N \times C_L$$

$$t_{pLH} = 0.69 R_P \times C_L$$

- 利用一阶RC延迟分析方法

$$t_{pHL} = f(R_N \times C_L)$$


$$t_{pHL} = 0.69 R_N \times C_L$$

$$t_{pLH} = 0.69 R_P \times C_L$$

- Keep capacitances small – lower C
 - Compact layout, good placement (short wires & no diffusion routing)
- Increase transistor sizes – lower R
 - Watch out for self-loading! – parasitic C increases!
- Increase VDD
 - Not usually possible due to reliability and power penalties

输入Pattern对延迟的影响


- 利用一阶RC延迟分析方法

 


- Delay is dependent on the **pattern** of inputs
- *Ignore C_{int} for the moment!*
- Low to high transition
 - both inputs go low
 - delay is $0.69 R_p/2 C_L$
 - one input goes low
 - delay is $0.69 R_p C_L$
- High to low transition
 - both inputs go high
 - delay is $0.69 2R_n C_L$

利用Transistor Ordering提升逻辑速度

- 复杂的Transistor Ordering需要仿真工具支持

 

 delay determined by time to
discharge C_L , C_1




delay determined by time to
discharge C_L


作业题

逻辑电路的Transistor Sizing

- 目标是将PDN和PUN的延迟进行匹配


 


 - Delay is dependent on the **pattern** of inputs
- *Ignore C_{int} for the moment!*
- Low to high transition
 - both inputs go low
 - delay is $0.69 R_p / 2 C_L$
 - one input goes low
 - delay is $0.69 R_p C_L$
- High to low transition
 - both inputs go high
 - delay is $0.69 2R_n C_L$



逻辑电路的Transistor Sizing

- 目标是将PDN和PUN的延迟进行匹配

  


$$OUT = D + A \cdot (B + C)$$

• 拓展多级的RC模型

- ON transistors look like resistors
- Circuit network modeled as *RC ladder*
- Elmore delay of RC ladder
- Apply to complex gates (i.e., stacks), also interconnect (later)

$$t_{pd} \approx \sum_{\text{nodes } i} R_{i-to-source} C_i$$

 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



逻辑电路的Elmore Delay模型

拓展多级的RC模型 – 3-input NAND gates

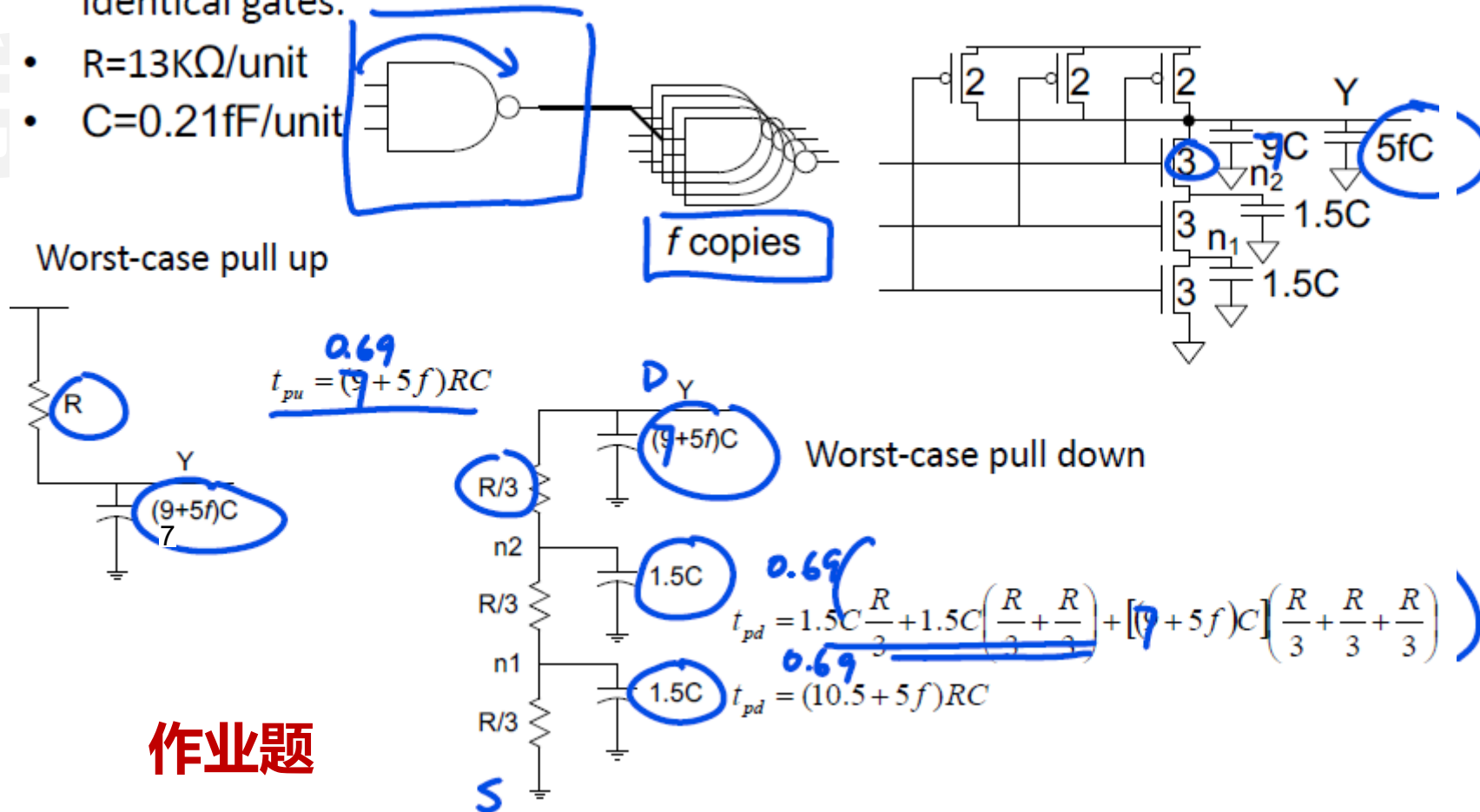- Estimate worst-case rising and falling delay of 3-input NAND driving f identical gates.
- $R=13\text{K}\Omega/\text{unit}$
- $C=0.21\text{fF}/\text{unit}$



作业题

引入逻辑功效

- 最基本的问题：如何对一串逻辑门电路进行Transistor Sizing以最小化延时？

逻辑门电路的延迟: $d = f + p$

- f : effort delay = gh (a.k.a. stage effort)

– Again has two components

- g : logical effort

– Measures relative ability of gate to deliver current

– $g \approx 1$ for inverter

- h : electrical effort = C_{out} / C_{in}

– Ratio of output to input capacitance


– Sometimes called fanout

- p : parasitic delay

– Represents delay of gate driving no load


– Set by internal parasitic capacitance
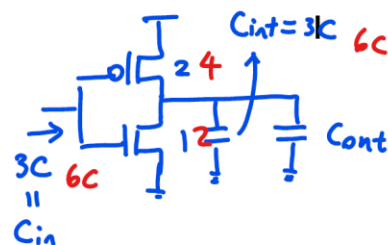
$$d = t_p / \tau \quad t \sim 9\text{ps in typical 130nm process}$$



$$t_p = 0.69 R(3C + C_{int}) \\ = 0.69(3RC) + 0.69RC_{int}$$
 
$$d = 1 + \frac{C_{out}}{3C} \\ = \frac{C_{out}}{C_{in}} + 1 \\ = gh + p \quad (p=1)$$



- Reference is the inverter:

$$g_{inv} = 1$$

$$p_{inv} = 1$$

- g is a function of the complexity of a gate, not its size

- p is a function of the technology and gate type

- $\tau \sim 9\text{ps}$ in typical 130nm process


$$d = f + p \\ = gh + p \\ = h + p$$

$$t_p = 0.69 \cdot \frac{R}{2} (6C + C_{out}) \\ = 0.69(3RC) + 0.69 \frac{R}{2} C_{out} \\ d = 1 + \frac{C_{out}}{6C} \\ = \frac{C_{out}}{C_{in}} + 1 \\ = gh + p \quad (p=1)$$


不同逻辑门电路的Logical Effort (g)

- 最基本的问题：如何对一串逻辑门电路进行Transistor Sizing以最小化延时？

 
- DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current (i.e., effort delay under same loading).*
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

不同逻辑门电路的Logical Effort (g)

- 最基本的问题：如何对一串逻辑门电路进行Transistor Sizing以最小化延时？


Logical effort (g)

Gate type	Number of inputs					
	1	2	3	4	5	n
Inverter	1					
NAND		$4/3$	$5/3$	$6/3$	$7/3$	$(n + 2)/3$
NOR		$5/3$	$7/3$	$9/3$	$11/3$	$(2n + 1)/3$
Multiplexer		2	2	2	2	2


不同逻辑门电路的寄生延迟 (p)

- 最基本的问题：如何对一串逻辑门电路进行Transistor Sizing以最小化延时？

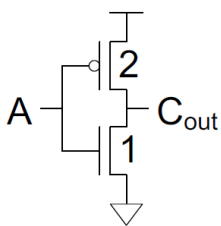
- Measure from delay vs. fanout plots
- Or estimate by counting self loading on output node for sizing with equal output current to inverter
- For simplification, we ignore internal node capacitance



$$C_{out} = 3$$
$$p = 3/3$$

 

$$C_{out} = 6$$
$$p = 6/3 = 2$$

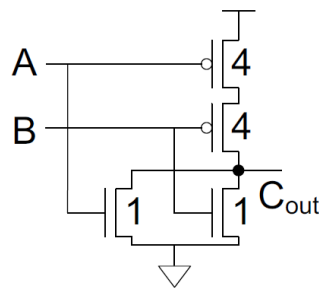


$$C_{out} = 6$$
$$p = 6/3 = 2$$

Gate type	Parasitic Delay
Inverter	1
n-input NAND	n
n-input NOR	n
n-way multiplexer	2n

利用逻辑功效计算电路延迟

- 单级 - 反相器FO4经典例子与复杂逻辑例子

 


$$C_{out} = 4C_{in}$$

$$h = 4$$

$$g = 1$$

$$p = 1$$

$$D = 4 + 1 = 5\tau$$

 

$$h = 3$$

$$g = \frac{6}{3}$$


$$p = 4 \times 1$$

$$D = 10\tau$$

主讲：陶耀宇、李萌

利用逻辑功效计算电路延迟

• 多级电路延迟计算

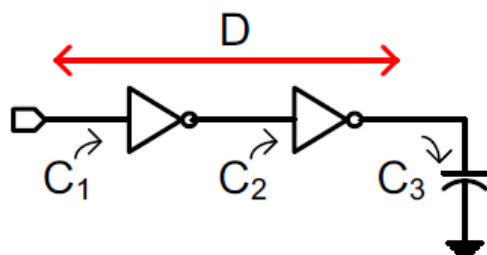


Define path effort H as:

$$H = \frac{C_3}{C_1}$$

$$h_1 = \frac{C_2}{C_1}$$

$$h_2 = \frac{C_3}{C_2}$$

$$H = h_1 h_2$$

 

Without branching: $h_1 h_2 = H$

With branching: $h_2 = \frac{C_3}{C_2}$

$$h_1 = \frac{3C_2}{C_1}$$

$$h_1 h_2 = 3H$$

Need to account for branching!

$$b_i = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$$

$$C_{on-path,2} = C_2$$

$$C_{off-path,2} = 2C_2$$

$$b_1 = \frac{3C_2}{C_2} = 3$$

利用逻辑功效计算电路延迟

• 多级电路延迟计算

$$H = \frac{C_{out}}{C_{in}}$$

$$B = \prod b_i$$

$$BH = \prod h_i$$

$$G = \prod g_i$$

$$P = \sum p_i$$

Path Effort

$$F = GBH = \prod \underline{g_i h_i}$$

Total delay $D = g_1 h_1 + p_1 + g_2 h_2 + p_2$

Substitute H $D = g_1 h_1 + p_1 + g_2 \frac{H}{h_1} + p_2$

$$\min\{D\} \Rightarrow \frac{\partial D}{\partial h_1} = g_1 - g_2 \frac{H}{h_1^2} = 0$$

Minimize the delay


$$g_1 - g_2 \frac{h_2}{h_1} = 0$$

Solve for the minimum delay

$$g_1 h_1 = g_2 h_2$$

$$f_1 = f_2$$

 Delay is optimal when effort delays are equal



利用逻辑功效计算电路延迟


Logical effort (g)



- 多级电路延迟计算例子

Gate type	Number of inputs					
	1	2	3	4	5	n
Inverter	1					
NAND		4/3	5/3	6/3	7/3	(n + 2)/3
NOR		5/3	7/3	9/3	11/3	(2n + 1)/3
Multiplexer		2	2	2	2	2

Minimum Delay

 

Stage effort of stage i: f_i

$$g_i h_i = f_i$$

Optimal stage effort is:

$$\hat{f} = f_i$$

For N stages:

$$F = \hat{f}^N \Rightarrow \hat{f} = F^{1/N}$$

Minimum Delay:

$$\hat{D} = \sum_i g_i h_i + p_i$$

$$\hat{D} = N\hat{f} + \sum_i p_i = N\hat{f} + P$$

$$G = g_a g_b g_c = (4/3)^3 = 2.37$$

$$B = 1$$

$$H = C_L / C_{in} = 27$$

$$F = GBH = 2.37 \times 27 = 63.99$$

$$\hat{f} = F^{1/3} \approx 4$$

$$\hat{D} = 3(4) + 3(2p_{inv}); p_{inv} = 1\tau$$

$$\hat{D} = 12 + 6 \times 1 = 18\tau$$

利用逻辑功效计算电路延迟

Logical effort (g)



- 多级电路延迟计算例子

Gate type	Number of inputs					
	1	2	3	4	5	n
Inverter	1					
NAND		4/3	5/3	6/3	7/3	(n + 2)/3
NOR		5/3	7/3	9/3	11/3	(2n + 1)/3
Multiplexer		2	2	2	2	2



Compute: $\hat{f} = g \cdot h$

$$h_i = \hat{f} / g_i = C_{out} / C_{in}$$

$$C_{in} = \frac{g_i C_{out}}{\hat{f}}$$

$C_{out} = \frac{\hat{f} C_{in}}{g_i}$

Work backwards to size each gate

 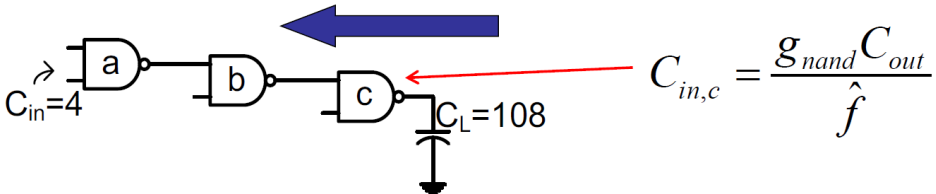


$$C_{in,c} = \frac{g_{nand} C_{out}}{\hat{f}}$$

$$C_{in,c} = \frac{4/3 \times 108}{4} = 36$$

$$C_{in,b} = \frac{4/3 \times 36}{4} = 12$$

$$C_{in,a} = \frac{4/3 \times 12}{4} = 4$$

 Check work by verifying input cap spec is met!



$$C_{in} = \frac{2}{4} \times 36$$

$$C_{in} = 18$$

作业题

目 录


CONTENTS



- 01. 晶体管与逻辑门电路基础**
- 02. 电路延迟分析与逻辑功效**
- 03. 动态逻辑电路与时序电路**
- 04. 复杂计算单元与线路分析**

基本的Domino逻辑门电路

- 利用时钟将逻辑计算分为预充电和计算两步

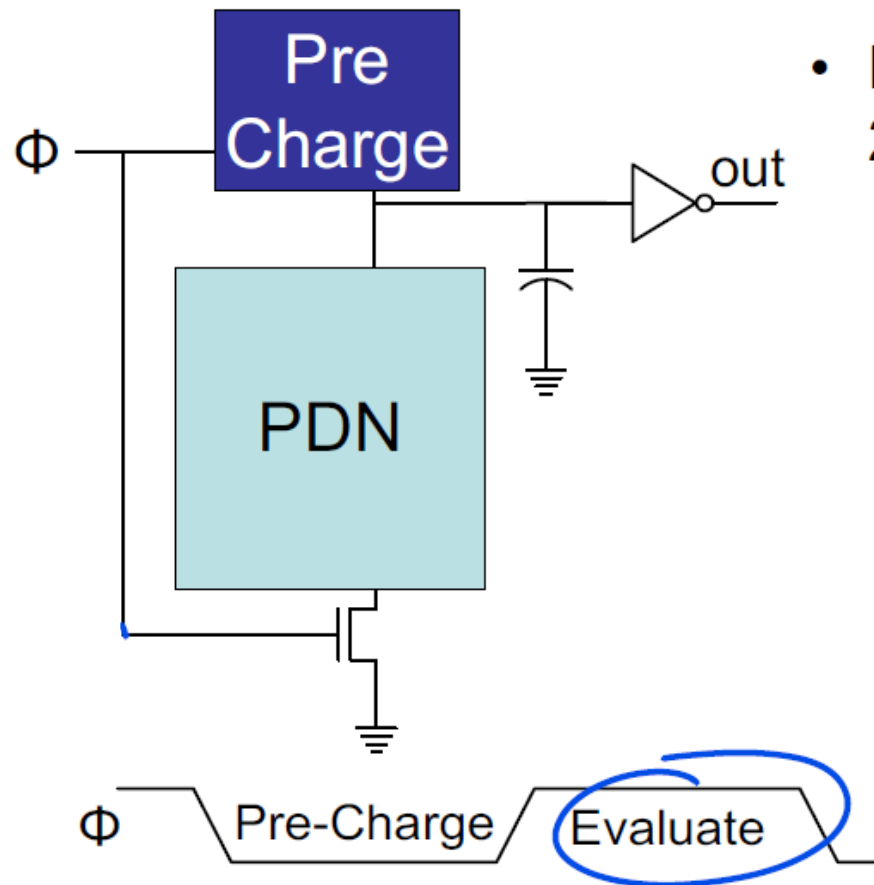


- Divide the clock in 2 phases:
 - Precharge
 - Output Low
 - Dyn. cap precharge
 - PDN Off
 - Evaluate
 - Conditional discharge
 - Input must be stable and monotonic $L \rightarrow H$

Domino逻辑门电路的好处


- 对于复杂的电路逻辑，能够大幅降低Logical Effort从而降低电路延迟

3-input OR gate

 

Static:
 $C_i = 7$
 $C_n = 9$

$$g_i = \frac{7}{3}$$

 

Skew for eval



Dynamic:
 $C_i = 2$
 $C_n = 7$

$$g_i = \frac{2}{3}$$


- Advantages:
 - Faster than CMOS
 - Input capacitance is lower
 - Early switch point
 - Inverter P/N > 2 (only rising delay important)

Domino逻辑门电路的问题

- 漏电流问题 (Leakage) 和输入保持时间问题

  

 First gate in domino chain $\uparrow$ delay




Dynamic node is floating during evaluation

– Leakage current of NMOS can discharge it

输入保持时间需要够长


Domino Cascading

- **Domino逻辑门的多级互连**

 

Footless Domino


- Domino逻辑门的多级互连

 

- Advantages:

- Faster than classic domino → one less NMOS
 - Why is footer necessary in the first stage?
 - Input not guaranteed during precharge

- 同步时序 (Synchronous Timing)

 


触发器
(Register)

组合逻辑 (各种逻辑门电路)


电路时序的基本概念

- 触发器的Setup Time和Hold Time

 



Setup Time

Hold Time

 

• 同步时序 (Synchronous Timing)

Timing Metrics


 
 


$$T_{c-q} + t_{plogic, \min} \geq t_{hold}$$

$$T \geq t_{c-q} + t_{plogic, \max} + t_{su}$$

电路时序的基本概念

• 时钟的不稳定性

   

Minimum cycle time:

$$T \geq t_{c-q} + t_{su} + t_{logic} - \delta$$

Worst case is when receiving edge arrives early (negative δ)

作业题

Hold time constraint:

$$t_{(c-q, cd)} + t_{(logic, cd)} > t_{hold} + \delta$$

Worst case is when receiving edge arrives late (positive skew)

Race between data and clock

cd: contamination delay (fastest possible delay)

目 录


CONTENTS



 
- 01. 晶体管与逻辑门电路基础**
- 02. 电路延迟分析与逻辑功效**
- 03. 动态逻辑电路与时序电路**
- 04. 复杂计算单元与线路分析**

• 简单1bit加法器电路

- $C_o = AB + BC_i + AC_i = AB + (A + B)C_i$
- $S = A \oplus B \oplus C_i = ABC_i + \overline{C_o}(A + B + C_i)$
- 28 transistors



- Ripple Carry加法器电路

 


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{adder} = (N-1)t_{carry} + t_{sum}$$

Goal: Make the fastest possible carry path circuit

• 基于PGK的加法器设计方法

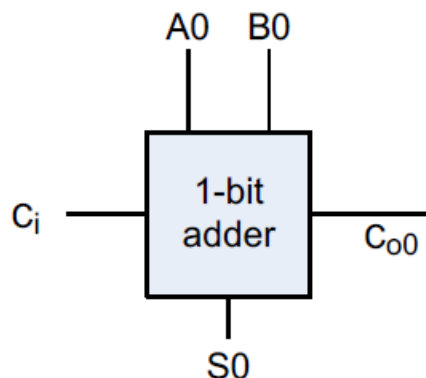

Generate (G) = AB

Propagate (P) = $A \oplus B$

– Generate: $C_{out} = 1$ independent of C_{in}

- $G = A \cdot B$

– Propagate: $C_{out} = C_{in}$

- $P = A \oplus B$

– Kill: $C_{out} = 0$ independent of C_{in}

- $K = \sim A \cdot \sim B$

$$C_o(G, P) = \underline{G + PC_i} \rightarrow \begin{cases} P = A \oplus B \\ P = A + B \end{cases}$$
$$S(G, P) = P \oplus C_i$$

• 基于PGK的加法器设计方法


Carry-Ripple using P and G

$$C_{i:0} = G_i + P_i \cdot C_{i-1:0}$$

$$G_{0:0} = C_{in}$$

$$P_{0:0} = 0$$

$$C_{out,i} = G_{i:0}$$

 

$$C_{0,1} = G_1 + P_1 C_{in}$$


$$C_{0,2} = G_2 + P_2 C_{0,1}$$

$$G_{1:0} = G_1 + P_1 G_0$$


$$G_{2:0} = G_2 + P_2 G_{1:0}$$

$$t_{adder} = t_{setup} + (N-1) t_{carry} + \max(t_{carry}, t_{sum})$$

- 基于PGK的加法器设计方法

 


PG生成逻辑

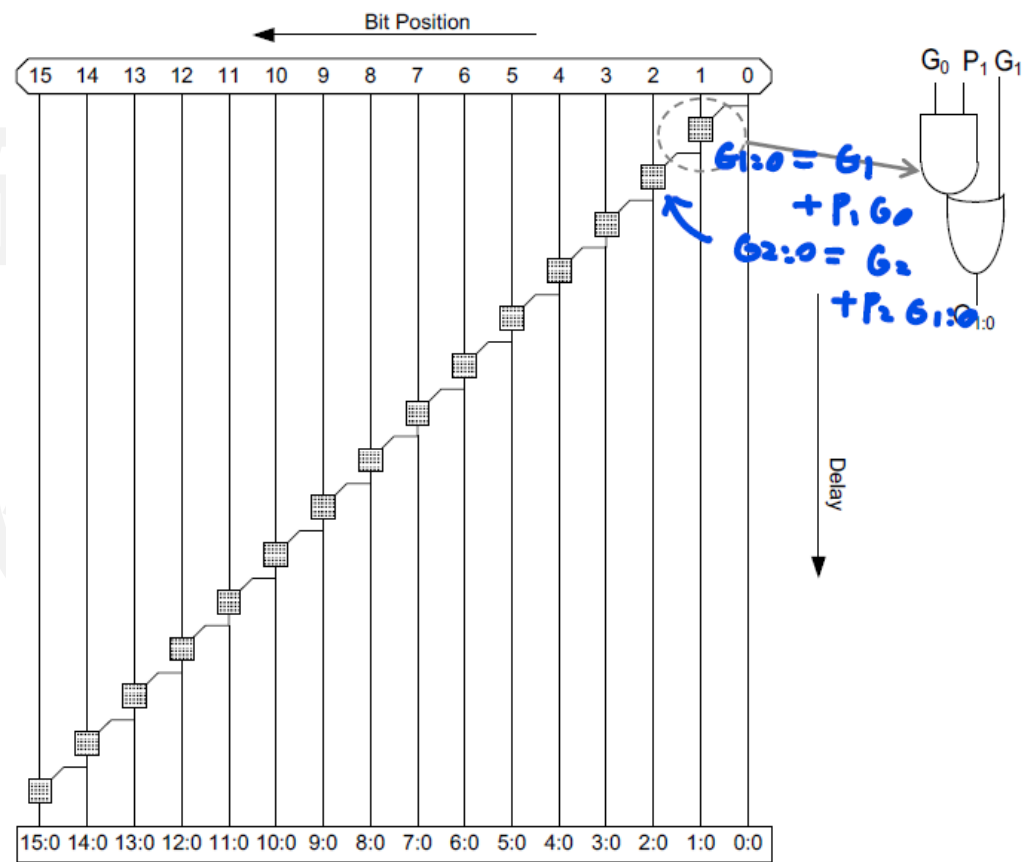

Carry Ripple的PG图

• 基于PGK的加法器设计方法 – 复杂PG树加法器

 

$\log_2(N)$

$$G_{13:0} = G_{13:6} + P_{13:6} G_{5:0}$$

$$\begin{cases} G_{13:6} = G_{13:10} + P_{13:0} G_{9:6} \\ P_{13:6} = P_{13:10} P_{9:6} \end{cases}$$

$$G_{5:0} = G_{5:2} + P_{5:2} G_{1:0}$$




作业题

加法器设计


• 基于PGK的加法器设计方法 – 复杂PG树加法器

Brent-Kung

 


$\log_2(n)$

Sklansky

 

- Uneven sizing (10:8) + (7:0)
- Large fanout

Han-Carlson

 

- Kogge-Stone: low logic levels, low fanout, high wiring
- Brent-Kung: low fanout, low wiring, high logic levels
- Sklansky: low logic levels, low wiring, high fanout

- 乘法器设计的核心是部分和累加

Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline 00111100 : 60_{10} \end{array}$$

multiplicand

multiplier

partial
products

product

M x N-bit multiplication

- Produce N M-bit partial products
- Sum these to produce M+N-bit product

- 乘法器设计的核心是部分和累加

Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$

Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

Product:
$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$


							y_5	y_4	y_3	y_2	y_1	y_0
							x_5	x_4	x_3	x_2	x_1	x_0
							x_0y_5	x_0y_4	x_0y_3	x_0y_2	x_0y_1	x_0y_0
						x_1y_5	x_1y_4	x_1y_3	x_1y_2	x_1y_1	x_1y_0	
					x_2y_5	x_2y_4	x_2y_3	x_2y_2	x_2y_1	x_2y_0		
				x_3y_5	x_3y_4	x_3y_3	x_3y_2	x_3y_1	x_3y_0			
			x_4y_5	x_4y_4	x_4y_3	x_4y_2	x_4y_1	x_4y_0				
		x_5y_5	x_5y_4	x_5y_3	x_5y_2	x_5y_1	x_5y_0					
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	

multiplicand
multiplier

partial
products

product



Each dot represents a bit

 

乘法器设计

- 乘法器设计的核心是部分和累加

Each dot represents a bit

  

• 如何减少部分和累加的次数?

- Array multiplier requires N partial products
- If we looked at groups of r bits, we could form N/r partial products.

$\begin{array}{r} x \\ (0\ 0) \\ (0\ 1) \\ (1\ 0) \\ (1\ 1) \end{array}$

- Faster and smaller?
- Called radix- 2^r encoding

Ex: $r = 2$: look at pairs of bits

– Form partial products of $0, Y, 2Y, 3Y$

– First three are easy, but $3Y$ requires adder ☹

$3Y = (4Y - Y)$

	1	1	0	0
	(0	1)	(0	1
	a	a	a	a
b	b	b	b	

• 如何减少部分和累加的次数 – 布斯编码 (Radix-2^r)

- Instead of 3Y, try -Y, then increment next partial product to add 4Y
- Similarly, for 2Y, try -2Y + 4Y in next partial product

4Y - 2Y | 0

4Y - Y | 1

Inputs			Partial Product	Booth Selects		
x_{2i+1}	x_{2i}	x_{2i-1}	PP_i	SINGLE _i	DOUBLE _i	NEG _i
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0	Y	1	0	0
0	1	1	2Y	0	1	0
1	0	0	-2Y	0	1	1
1	0	1	-Y	1	0	1
1	1	0	-Y	1	0	1
1	1	1	-0 (= 0)	0	0	1

Y

-Y


Y

作业题


- Shifter也是重要的数字电路模块之一

```
module barrel_shifter
(
    input logic [7:0] a,
    input logic [2:0] amt,
    output logic [7:0] y
);

 always_comb
    case (amt)
        3'b000: y = a;
        3'b001: y = {a[0], a[7:1]};
        3'b010: y = {a[1:0], a[7:2]};
        3'b011: y = {a[2:0], a[7:3]};
        3'b100: y = {a[3:0], a[7:4]};
        3'b101: y = {a[4:0], a[7:5]};
        3'b110: y = {a[5:0], a[7:6]};
        3'b111: y = {a[6:0], a[7]};
        default: y = a;
    endcase
endmodule
```




• Wire Geometry

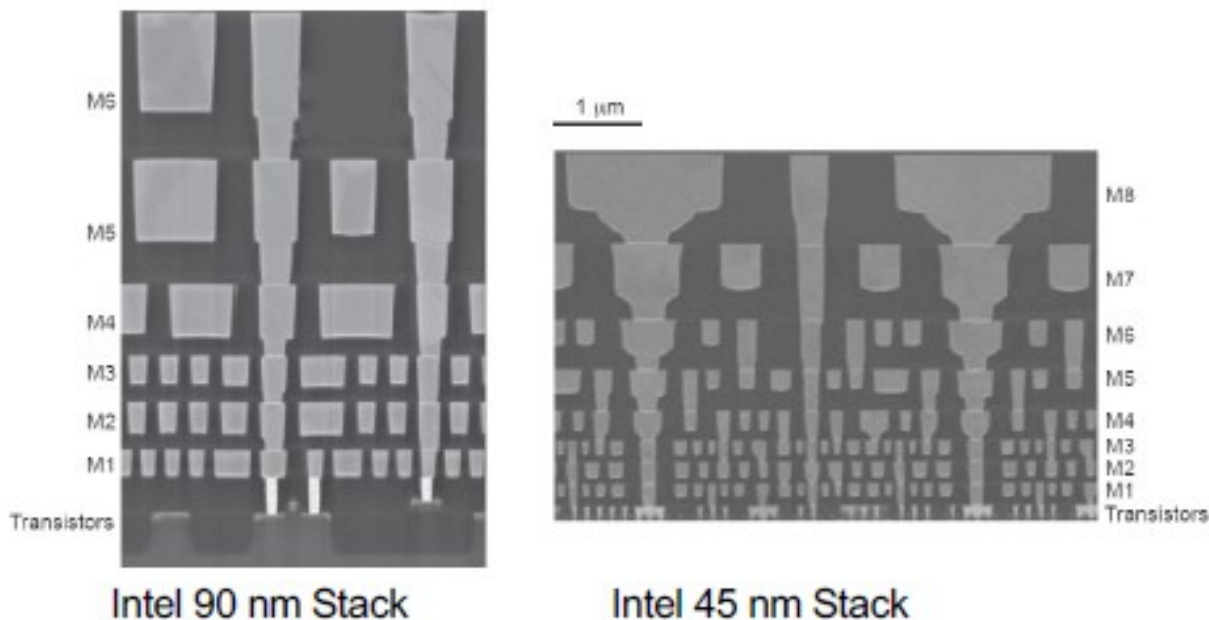


线电阻的计算方式

 - $\rho = \text{resistivity } (\Omega \cdot \text{m})$
$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$
- $R_{\square} = \text{sheet resistance } (\Omega/\square)$
 - $\square$ is a dimensionless unit(!)
- Count number of squares
 - $R = R_{\square} * (\# \text{ of squares})$





• Wire Repeaters

 - R and C are proportional to l
- RC delay is proportional to l^2
 - Unacceptably great for long wires
- Break long wires into N shorter segments
 - Drive each one with an inverter or buffer



- How many repeaters should we use?
- How large should each one be?
- Equivalent Circuit

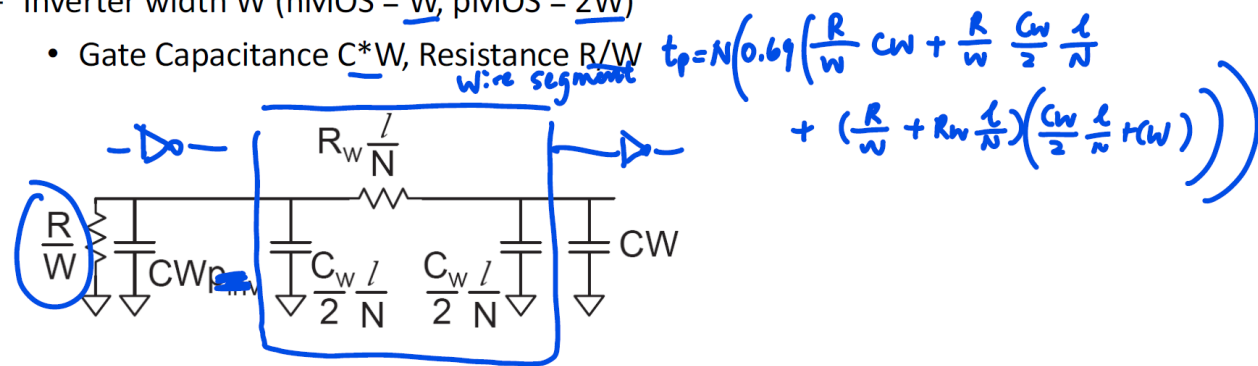 - Wire length l/N
 - Wire Capacitance $C_w * l/N$, Resistance $R_w * l/N$
- Inverter width W (nMOS = W , pMOS = $2W$)
 - Gate Capacitance $C * W$, Resistance R/W



• Wire Repeaters

- Write equation for Elmore Delay
 - Differentiate with respect to W and N
 - Set equal to 0, solve

$$\underbrace{\frac{l}{N}}_{\text{unit wire segment}} = \sqrt{\frac{2RC'}{R_w C_w}} \quad \begin{array}{l} \text{unit inv resistance} \\ \text{unit inv cap} \end{array}$$

$C' = C(1 + p_{\text{inv}})$

R_w unit wire res

$$W = \sqrt{\frac{RC_w}{R_w C'}}$$

作业题