

6. Logical Effort

Jacob Abraham

Department of Electrical and Computer Engineering
The University of Texas at Austin

VLSI Design
Fall 2020

September 15, 2020

Calculate the Elmore delay from C to F in the circuit. The widths of the pass transistors are shown, and the inverters have minimum-sized

Use the Elmore delay approximation to find the *worst-case* rise and fall delays at output F for the following circuit. The gate sizes of the transistors are shown in the figure. Assume NO sharing of diffusion regions, and the worst-case conditions for the initial charge on a node.

Example: Delay with Different Input Sequences

Find the delays for the given input transitions (gate sizes shown in figure)


Assumptions: diffusion capacitance is equal to the gate capacitance, the resistance of an nMOS transistor with unit width is R and the resistance of a pMOS transistor with width 2 is also R , and NO sharing of diffusion regions

Off-path capacitances can contribute to delay, and if a node does not need to be charged (or discharged), its capacitance can be ignored

$$ABCD = 0101 \rightarrow ABCD = 1101$$

$$ABCD = 1111 \rightarrow ABCD = 0111$$

$$ABCD = 1010 \rightarrow ABCD = 1101$$

 

Delay with Different Input Sequence, Cont'd

Look at the charges on the nodes at the end of the first input of the sequence; only the capacitances of the nodes which would change with the second vector need to be considered

$$ABCD = 0101 \rightarrow$$

$$ABCD = 1101;$$

$$\text{Delay} = 36RC$$

$$ABCD = 1111 \rightarrow$$


$$ABCD = 0111;$$

$$\text{Delay} = 16RC$$

$$ABCD = 1010 \rightarrow$$

$$ABCD = 1101;$$

$$\text{Delay} = 43RC$$

 

Delay Components

Delay has two parts

Parasitic Delay

- 6 or 7 RC
- Independent of Load



Effort Delay

- 4h RC
- Proportional to load capacitance

Contamination Delay

Minimum (Contamination) Delay

  - Best-case (contamination) delay can be substantially less than propagation delay
- Example, If both inputs fall simultaneously
- Important for “hold time” (will see later in the course)



$$t_{cdr} = (3 + 2h)RC$$

Introduction to Logical Effort

Chip designers have to face a bewildering array of choices

- What is the best circuit topology for a function?
- How many stages of logic give least delay?
- How wide should the transistors be?

Logical effort is one method to make these decisions

- Uses a simple model of delay
- Allows back-of-the-envelope calculations
- Helps make rapid comparisons between alternatives
- Emphasizes remarkable symmetries

Example


Design the decoder for a register file

Decoder specifications

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors

Need to decide

 - How many stages to use?
- How large should each gate be?
- How fast can decoder operate?



Delay in a Logic Gate

Express delay in a process-independent unit

$$\tau = 3RC$$

$$d = \frac{d_{abs}}{\tau}$$

≈ 12 ps in 180 nm process

40 ps in 0.6 μm process

Delay has two components: $d = f + p$

Effort delay, $f = gh$ (stage effort)

g: Logical Effort

Measures relative ability of gate to deliver current

$g \equiv 1$ for inverter

h: Electrical Effort = C_{out}/C_{in}

Ratio of output to input capacitances, sometimes called fanout effort


Parasitic delay, p

- Represents delay of gate driving no load
- Set by internal parasitic capacitance

Delay Plots


$$\begin{aligned}d &= f + p \\ &= gh + p\end{aligned}$$

What about
NOR2?

 


Computing Logical Effort

 
- **Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current**
- Measure from delay vs. fanout plots
- Or, estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

- **Logical Effort of common gates**


Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate/Mux	2	2	2	2	2
XOR, XNOR		4,4	6,12,6	8,16,16,8	

- **Parasitic delay of common gates**
 - In multiples of $p_{inv} (\approx 1)$

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate/Mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: Ring Oscillator

Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g = 1$

Electrical Effort: $h = 1$

Parasitic Delay: $p = 1$


Stage Delay: $d = 2$

Frequency: $f_{osc} = 1/(2 \cdot N \cdot d) = 1/4N$

31 stage ring oscillator in 0.6 μm process has frequency of ~ 200 MHz

 Example: FO4 Inverter

Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$
Electrical Effort: $h = 4$
Parasitic Delay: $p = 1$
Stage Delay: $d = 5$

The FO4 delay is about:
200 ps in a $0.6\mu\text{m}$ process
60 ps in a 180 nm process
 $f/3$ ns in a $f\ \mu\text{m}$ process
($f/3$ ps in a f nm process)

Example Problem

A particular technology node has a FO4 delay of 9 ps. How many minimum size (2:1) inverters need to be included in a ring oscillator so that the frequency is close to 7.3 GHz?

$$\text{FO4 delay} = 15RC = 9ps$$

$$\text{Stage delay} = 6RC = 3.6ps$$


$$f = \frac{1}{2 \times N \times d} \implies$$

$$\begin{aligned} N &= \frac{1}{2 \times f \times d} \\ &= \frac{1}{2 \times 7.3 \times 3.6 \times 10^{-3}} \\ &= 19.05 \end{aligned}$$

Number of inverters = 19

Multistage Logic Networks

 - Logical effort generalizes to multistage networks
- **Path Logical Effort**, $G = \prod g_i$
- **Path Electrical Effort**, $H = \frac{C_{out-path}}{C_{in-path}}$
- **Path Effort**, $F = \prod f_i = \prod g_i h_i$



- Can we write $F = GH$ in general?

Consider Paths that Branch

$$G = 1$$


$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

 

Branching Effort and Multistage Delays

Branching Effort accounts for branching between stages in path

$$b = \frac{C_{on\ path} + C_{off\ path}}{C_{on\ path}}$$

$$B = \prod b_i \quad (\text{Note : } \prod h_i = BH)$$

Now, path effort, $F = GBH$

Multistage Delays

$$\text{Path Effort Delay, } D_F = \sum f_i$$

$$\text{Path Parasitic Delay, } P = \sum p_i$$

$$\text{Path Delay, } D = \sum d_i = D_F + P$$

$$D = \sum d_i = D_F + P$$

Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

Thus, the minimum delay of an N-stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

How wide should the gates be for the least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\implies C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives
- Check work by verifying input capacitance specification is met

 Example: 3-stage Path

Select gate sizes x and y for least delay from A to B



Example: 3-stage Path, Cont'd

 


Logical Effort	$G = (4/3) * (5/3) * (5/3) = 100/27$
Electrical Effort	$H = 45/8$
Branching Effort	$B = 3 * 2 = 6$
Path Effort	$F = GBH = 125$
Best Stage Effort	$\hat{f} = \sqrt[3]{F} = 5$
Parasitic Delay	$P = 2 + 3 + 2 = 7$
Delay	$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$

Example: 3-stage Path, Cont'd

Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$

$$x = (15*2) * (5/3) / 5 = 10$$

 


Best Number of Stages

How many stages should a path use?

- Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter


$$D = NF^{\frac{1}{N}} + P$$

$$D = N(64)^{\frac{1}{N}} + N$$

 

Sensitivity Analysis

 
How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 - We can be sloppy
 - For example, use $\rho = 4$

Decoder Example: Number of Stages

 - 16 word, (32 bit) register file
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors



Find: number of stages, sizes of gates, speed

- Decoder effort is mainly electrical and branching
 - Electrical Effort: $H = (32 \cdot 3) / 10 = 9.6$
 - Branching Effort: $B = 8$
- If we neglect logical effort (assume $G = 1$)
 - Path Effort: $F = GBH = 76.8$
- Number of Stages: $N = \log_4 F = 3.1$
- Try a 3-stage design

Decoder: Gate Sizes and Delay

Logical Effort: $G = 1 * 6/3 * 1 = 2$


Path Effort: $F = GBH = 154$

Stage Effort: $\hat{f} = F^{\frac{1}{3}} = 5.36$

Path Delay: $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

Gate sizes: $z = 96 * 1 / 5.36 = 18$

Gate sizes: $y = 18 * 2 / 5.36 = 6.7$

 

Decoder: Comparison

Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

Review of Definitions

Term	Stage	Path
Number of stages	1	N
Logical effort	g	$G = \prod g_i$
Electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
Branching effort	$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}}$	$B = \prod b_i$
Effort	$f = gh$	$F = GBH$
Effort delay	f	$D_F = \sum f_i$
Parasitic delay	p	$P = \sum p_i$
Delay	$d = f + p$	$D = \sum d_i = D_F + P$

Method of Logical Effort

1. Compute path effort $F = GBH$
2. Estimate best number of stages $N = \log_4 F$
3. Sketch path with N stages
4. Estimate least delay $D = NF^{\frac{1}{N}} + P$
5. Determine best stage effort $\hat{f} = F^{\frac{1}{N}}$
6. Find gate sizes $C_{in} = \frac{g_i C_{out}}{f}$

Limits of logical effort

- Chicken and egg problem
 - Need path to compute G
 - But, don't know number of stages without G
- Simplistic delay model, neglects input rise time effects
- Interconnect
 - Iteration required in designs with significant wires
- Maximum speed only
 - Not minimum area/power for constrained delay

Summary of Logical Effort

Logical effort is useful for thinking of delay in circuits

- Numeric logical effort characterizes gates
- NANDs are faster than NORs in CMOS
- Paths are fastest when effort delays are ~ 4
- Path delay is weakly sensitive to stages, sizes
- But using fewer stages doesn't mean faster paths
- Delay of path is about $\log_4 F$ FO4 inverter delays
- Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits, but requires practice to master