



北京大学
PEKING UNIVERSITY


智能硬件体系结构

第三讲Supp：电路基础-晶体管与数字电路设计-2

潘泽伦

2024年秋季

• Hold Time Constraint

 


$$T_{c-q} + t_{plogic, \min} \geq t_{hold}$$

假设clk没有非理想特性:

- R1存着t时刻的值 x_t , R2存着t-1时刻的值 $f(x_{t-1})$ (因为clk同时到达R1与R2, 因此R2锁存上一时刻的R1输出经过组合逻辑值)
- t+1时刻clk到达, R1变为t+1时刻值 x_{t+1} , 为了使R2正确采样到 $f(x_t)$, x_t 经过组合逻辑之后的 $f(x_t)$ 需保持大于R2的 t_{hold} 时间 (假设时钟足够长, 时钟来之前R2输入已经是 $f(x_t)$, 因此setup肯定满足)
- 而 $f(x_t)$ 的最小保持时间由R1的clk引起输出变化的延迟 $t_{c \rightarrow q}$ 的最小值加上组合逻辑的最小延迟 $t_{plogic, \min}$ 决定
- 因此有Hold Constraint

• Setup Constraint

 


$$T \geq t_{c-q} + t_{plogic,max} + t_{su}$$

max

假设clk没有非理想特性:

- R1存着t时刻的值 x_t , R2存着t-1时刻的值 $f(x_{t-1})$ (因为clk同时到达R1与R2, 因此R2锁存上一时刻的R1输出经过组合逻辑值)
- t+1时刻clk到达, R1变为t+1时刻值 x_{t+1} , 为了使R2正确采样到 $f(x_t)$, 需要在t时刻之后R2输入变为 $f(x_t)$ 足够久, 也即大于setup时间 t_{su}
- t时刻时钟之后R2输入变为 $f(x_t)$ 距离t+1时钟上升沿的最小距离为: $T - t_{c \rightarrow q,max} - t_{plogic,max}$
(即一个时钟周期减去最长的延迟)
- 因此有Setup Constraint

• CLK skew和jitter的影响

 

Minimum cycle time:


$$T \geq t_{c-q} + t_{su} + t_{logic} - \delta$$

Worst case is when receiving edge arrives early (negative δ)

- 对setup情况最坏来说是R2的clk来的比R1早了（意味着R2的输入需要更早变化为正确值），此时clk skew为负数
- 假如skew是正数，意味着R2时钟到达比R1晚，反而对时钟周期条件更加宽松，所以在不等式中减去skew影响
- 因此有得到带有clk skew的setup constraint公式

主讲：陶耀子、李萌

• CLK skew和jitter的影响

 

Hold time constraint:

$$t_{(c-q, cd)} + t_{(logic, cd)} > t_{hold} + \delta$$

Worst case is when receiving edge arrives late (positive skew)

Race between data and clock

cd: contamination delay (fastest possible delay)

- 对hold来说最坏情况是R2时钟来的更晚（意味着R2输入需要保持更长的时间才能确保在R2时钟到来之后维持hold时间），此时skew为正数，也即R2输入变化的最小延迟需要减去skew（也即除去R2时钟晚来的这一段）后仍大于hold time才能保证R2的正确采样
- 因此有得到带有clk skew的hold constraint公式

- 为什么需要一种硬件描述语言

What is HDL, Verilog?

What is Verilog?

- ▶ Hardware Description Language - IEEE 1364-2005
 - ▶ Superseded by SystemVerilog - IEEE 1800-2009
- ▶ Two Forms
 1. Behavioral
 2. Structural
- ▶ It can be built into hardware. If you can't think of at least one (inefficient) way to build it, it might not be good.

Why do I care?

- ▶ We use Behavioral Verilog to do computer architecture here.
- ▶ Semiconductor Industry Standard (VHDL is also common, more so in Europe)

• 行为级Verilog与模块级Verilog

Behavioral vs. Structural

Behavioral Verilog

- ▶ Describes function of design
- ▶ Abstractions
 - ▶ Arithmetic operations
(+, -, *, /)
 - ▶ Logical operations
(&, |, ^, ~)

Structural Verilog

- ▶ Describes construction of design
- ▶ No abstraction
- ▶ Uses modules, corresponding to physical devices, for everything

Suppose we want to build an adder?

- 用Verilog语言构建一个1bit的加法器

Structural Verilog

 


Figure: 1-bit Full Adder

```
module one_bit_adder(
    input wire a,b,cin,
    output wire sum,cout);
    wire w_0,w_1,w_2;
    xor u0(w_0,a,b);
    xor u1(sum,w_0,cin);
    and u2(w_1,w_0,cin);
    and u3(w_2,a,b);
    or u4(cout,w_1,w_2);
endmodule
```

Behavioral Verilog

```
module one_bit_adder(
    input wire a,b,cin,
    output wire sum,cout);
    assign sum = a ^ b ^ cin;
    assign cout = ((a ^ b) & cin) | a & b;
endmodule
```

OR ...

```
module one_bit_adder(
    input logic a,b,cin,
    output logic sum,cout);

    always_comb
    begin
        sum = a ^ b ^ cin;
        cout = 1'b0;
        if ((a ^ b) & cin) | (a & b))
            cout = 1'b1;
    end
endmodule
```

• 数据结构与可综合性

Data Types, Values

Synthesizable Data Types

`wires` Also called nets

```
wire a_wire;  
wire [3:0] another_4bit_wire;
```

- ▶ Cannot hold state

`logic` Replaced `reg` in SystemVerilog

```
logic [7:0] an_8bit_register;  
reg a_register;
```

- ▶ Holds state, might turn into flip-flops
- ▶ Less confusing than using `reg` with combinational logic (coming up...)

Unsynthesizable Data Types

`integer` Signed 32-bit variable

`time` Unsigned 64-bit variable

`real` Double-precision floating point variable

Four State Logic

0 False, low

1 True, high

Z High-impedance, unconnected net

X Unknown, invalid, don't care

运算符与赋值规则

Operators

Arithmetic	
*	Multiplication
/	Division
+	Addition
-	Subtraction
%	Modulus
**	Exponentiation
Bitwise	
~	Complement
&	And
	Or
~	Nor
^	Xor
^^	Xnor
Logical	
!	Complement
&&	And
	Or

Shift	
>>	Logical right shift
<<	Logical left shift
>>>	Arithmetic right shift
<<<	Arithmetic left shift
Relational	
>	Greater than
>=	Greater than or equal to
<	Less than
<=	Less than or equal to
!=	Inequality
!==	4-state inequality
==	Equality
===	4-state equality
Special	
{,}	Concatenation
{n{m}}	Replication
?:	Ternary

Setting Values

assign Statements

- ▶ One line descriptions of combinational logic
- ▶ Left hand side must be a wire (SystemVerilog allows assign statements on logic type)
- ▶ Right hand side can be any one line verilog expression
- ▶ Including (possibly nested) ternary (?:)

Example

```
module one_bit_adder(  
    input wire a,b,cin,  
    output wire sum,cout);  
    assign sum = a ^ b ^ cin;  
    assign cout = ((a ^ b) & cin) | a & b;  
endmodule
```

• 运算符与赋值规则

Setting Values

always Blocks

- ▶ Contents of always blocks are executed whenever anything in the sensitivity list happens
- ▶ Two main types in this class...
 - ▶ always_comb
 - ▶ implied sensitivity lists of every signal inside the block
 - ▶ Used for combinational logic. Replaced always @*
 - ▶ always_ff @(posedge clk)
 - ▶ sensitivity list containing only the positive transition of the clk signal
 - ▶ Used for sequential logic
- ▶ All left hand side signals need to be logic type.

Examples

Combinational Block

```
always_comb
begin
    x = a + b;
    y = x + 8'h5;
end
```

Sequential Block

```
always_ff @(posedge clk)
begin
    x <= #1 next_x;
    y <= #1 next_y;
end
```

• 运算符与赋值规则

Blocking vs. Non-blocking statement

Blocking Assignment

- ▶ Combinational Blocks
- ▶ Each assignment is processed in order, earlier assignments block later ones
- ▶ Uses the = operator

vs.

Nonblocking Assignment

- ▶ Sequential Blocks
- ▶ All assignments occur "simultaneously," delays are necessary for accurate simulation
- ▶ Uses the <= operator

Blocking Example

```
always_comb  
begin  
    x = new_val1;  
    y = new_val2;  
    sum = x + y;  
end
```

- ▶ Behave exactly as expected
- ▶ Standard combinational logic

 


Figure: Timing diagram for the above example.

工研·阿维

• 运算符与赋值规则

Nonblocking Example

```
always_ff @(posedge clock)
begin
    x <= #1 new_val1;
    y <= #1 new_val2;
    sum <= #1 x + y;
end
```

- ▶ What changes between these two examples?
- ▶ Nonblocking means that sum lags a cycle behind the other two signals

 


Figure: Timing diagram for the above example.

Bad Example

```
always_ff @(posedge clock)
begin
    x <= #1 y;
    z = x;
end
```

- ▶ z is updated after x
- ▶ z updates on negedge clock

 


Figure: Timing diagram for the above example.



• 避免Latch的出现

Latches

- ▶ What is a latch?
 - ▶ Memory device without a clock
- ▶ Generated by a synthesis tool when a net needs to hold state without being clocked (combinational logic)
- ▶ Generally bad, unless designed in intentionally
- ▶ Unnecessary in this class

Latches

- ▶ Always assign every variable on every path
- ▶ This code generates a latch
- ▶ Why does this happen?

```
always_comb
begin
    if (cond)
        next_x = y;
end
```

To avoid unintentional latches

Possible Solutions to Latches

```
always_comb
begin
    next_x = x;
    if (cond)
        next_x = y;
end
```

```
always_comb
begin
    if (cond)
        next_x = y;
    else
        next_x = x;
end
```


• 时序逻辑与组合逻辑的可综合性

Keys to Synthesizability

- ▶ Remember – Behavioral Verilog implies no specific hardware design
- ▶ But, it has to be synthesizable
- ▶ Better be able to build it somehow

Combinational Logic

- ▶ Avoid feedback (combinatorial loops)
- ▶ Always blocks should
 - ▶ Be `always_comb` blocks
 - ▶ Use the blocking assignment operator =
- ▶ All variables assigned on all paths
 - ▶ Default values
 - ▶ `if(...)` paired with an `else`

Sequential Logic

Sequential Logic

- ▶ Avoid clock- and reset-gating
- ▶ Always blocks should
 - ▶ Be `always_ff @(posedge clock)` blocks
 - ▶ Use the nonblocking assignment operator, with a delay `<= #1`
- ▶ No path should set a variable more than once
- ▶ Reset all variables used in the block
- ▶ `//synopsys sync_set_reset "reset"`

• 控制与流程

Flow Control

All Flow Control

- ▶ Can only be used inside procedural blocks (always, initial, task, function)
- ▶ Encapsulate multiline assignments with begin...end
- ▶ Remember to assign on all paths

Synthesizable Flow Control

- ▶ if/else
- ▶ case

Unsynthesizable Flow Control

- ▶ Useful in testbenches
- ▶ For example...
 - ▶ for
 - ▶ while
 - ▶ repeat
 - ▶ forever

Synthesizable Flow Control Example

```
always_comb
begin
    if (muxy == 1'b0)
        y = a;
    else
        y = b;
end
```

The Ternary Alternative

```
wire y;
assign y = muxy ? b : a;
```

Casez Example

```
always_comb
begin
    casez(alu_op)
        3'b000: r = a + b;
        3'b001: r = a - b;
        3'b010: r = a * b;
        ...
        3'b1???: r = a ^ b;
    endcase
end
```

• 测试与验证

Testing

What is a test bench?

- ▶ Provides inputs to one or more modules
- ▶ Checks that corresponding output makes sense
- ▶ Basic building block of Verilog testing

Why do I care?

- ▶ Finding bugs in a single module is hard...
- ▶ But not as hard as finding bugs after combining many modules
- ▶ Better test benches tend to result in higher project scores

工研·阿

Intro to Testbench

Features of the Test Bench

- ▶ Unsynthesized
 - ▶ Remember unsynthesizable constructs? This is where they're used.
 - ▶ In particular, unsynthesizable flow control is useful in testbenches (e.g. for, while)
- ▶ Programmatic
 - ▶ Many programmatic, rather than hardware design, features are available e.g. functions, tasks, classes (in SystemVerilog)

A good test bench should, in order...

1. Declare inputs and outputs for the module(s) being tested
2. Instantiate the module (possibly under the name DUT for Device Under Test)
3. Setup a clock driver (if necessary)
4. Setup a correctness checking function (if necessary/possible)
5. Inside an initial block...
 - 5.1 Assign default values to all inputs, including asserting any available reset signal
 - 5.2 \$monitor or \$display important signals
 - 5.3 Describe changes in input, using good testing practice

• Testbench的initial block

initial Block Example

```
initial
begin
    @(negedge clock);
    reset = 1'b1;
    in0 = 1'b0;
    in1 = 1'b1;
    @(negedge clock);
    reset = 1'b0;
    @(negedge clock);
    in0 = 1'b1;
    ...
end
```

task Example

```
task exit_on_error;
    input [63:0] A, B, SUM;
    input C_IN, C_OUT;
    begin
        $display("### Incorrect at time %4.0f", $time);
        $display("### Time:%4.0f clock:%b A:%h B:%h CIN:%b SUM:%h"
            "COUT:%b", $time, clock, A, B, C_IN, SUM, C_OUT);
        $display("### expected sum=%b", (A+B+C_IN) );
        $finish;
    end
endtask
```

Testbench常用组成模块

task

- ▶ Reuse commonly repeated code
- ▶ Can have delays (e.g. #5)
- ▶ Can have timing information (e.g. @(negedge clock))
- ▶ Might be synthesizable (difficult, not recommended)

function

- ▶ Reuse commonly repeated code
- ▶ No delays, no timing
- ▶ Can return values, unlike a task
- ▶ Basically combinational logic

function Example

```
function check_addition;
    input wire [31:0] a, b;
    begin
        check_addition = a + b;
    end
endfunction

assign c = check_addition(a,b);
```

• Testbench的示例

System tasks and functions

- \$monitor** Used in test benches. Prints every time an argument changes. Very bad for large projects.
e.g. `$monitor("format",signal,...)`
 - \$display** Can be used in either test benches or design, but not after synthesis. Prints once. Not the best debugging technique for significant projects.
e.g. `$display("format",signal,...)`
 - \$strobe** Like display, but prints at the end of the current simulation time unit.
e.g. `$strobe("format",signal,...)`
 - \$time** The current simulation time as a 64 bit integer.
 - \$reset** Resets the simulation to the beginning.
 - \$finish** Exit the simulator, return to terminal.
- More available at ASIC World.

Test Bench Setup

```
module testbench;  
    logic clock, reset, taken, transition, prediction;  
  
    two_bit_predictor(  
        .clock(clock),  
        .reset(reset),  
        .taken(taken),  
        .transition(transition),  
        .prediction(prediction));  
  
    always  
    begin  
        clock = #5 ~clock;  
    end
```

• Testbench内的testcase

Test Bench Test Cases

```
initial
begin
    $monitor("Time:%4.0f clock:%b reset:%b taken:%b trans:%b"
            "pred:%b", $time, clock, reset, taken,
            transition, prediction);
    clock = 1'b1;
    reset = 1'b1;
    taken = 1'b1;
    transition = 1'b1;
    @(negedge clock);
    @(negedge clock);
    reset = 1'b0;
    @(negedge clock);
    taken = 1'b1;
    @(negedge clock);
    ...
    $finish;
end
```

件体系结构

Remember to...

- ▶ Initialize all module inputs
- ▶ Then assert reset
- ▶ Use @(negedge clock) when changing inputs to avoid race conditions

李萌

• Verilog+Testbench的简单实例

```
module my_fir (
    input          clk,
    input          reset_n,
    input signed [7:0] fir_in,
    input          fir_val,
    output reg     fir_out_val,
    output reg signed [6:0] fir_out );

//=====
// Internal signals (wires and FFs)
//=====
localparam      h0      = -7;
localparam      h1      = 13;

...
reg             signed [7:0] in_d0;
reg             signed [7:0] in_d1;
...
reg             signed [7:0] in_d4;
Reg            in_val_reg;
wire            signed [11:0] mult_out0;
wire            signed [11:0] mult_out1;
...
wire            signed [14:0] sum_out;
...
assign          mult_out0 = in_d4*h0;      // combinational logic
assign          mult_out1 = in_d3*h1;

...
assign          sum_out = {{3, mult_out0[11]}, mult_out0} + {{3, mult_out1[11]}, mult_out1} + {{3, mult_out2[11]}, mult_out2} + {{3,
mult_out3[11]}, mult_out3} + {{3, mult_out4[11]}, mult_out4};      // sign extension and then add.
```

本例结构

```
always @(posedge clk or negedge reset_n)
begin
    if (~reset_n)
        begin
            in_d0      <= 0;
            in_d1      <= 0;
            ...
            in_val_reg      <= 1'b0;
            fir_out_val     <= 1'b0;
            fir_out        <= 0;
        end
    else
        begin
            in_val_reg      <= #1 fir_val;
            in_d0           <= #1 fir_in;
            in_d0           <= #1 in_d0;
            ...
            fir_out_val     <= #1 in_val_reg;
            fir_out         <= #1 sum_out[9:3];
        end
end
endmodule
```

• Verilog + Testbench的简单实例

```
`timescale 1 ns / 1 ps

module my_fir_tb;
parameter  CLOCK_PERIOD    = 125;    // 8MHz
reg        clk;
reg        reset_n;
reg signed [7:0]  fir_in;
reg        fir_val;
reg        fir_out_val;
reg signed [6:0]  fir_out;
integer      finput, in_read_cnt;

my_fir UUT(
    .clk      (clk      ),
    .reset_n  (reset_n  ),
    .fir_in   (fir_in   ),
    .fir_val  (fir_val  ),
    .fir_out  (fir_out  ),
    .fir_out_val (fir_out_val )
);
initial
begin
    finput      = $fopen("input.txt", "r");
    clk         = 1'b0;
    reset_n     = 1'b1;
    in_read_cnt = -1;
    #(CLOCK_PERIOD)
    reset_n     = 1'b0;
    #(CLOCK_PERIOD)
    reset_n     = 1'b1;
    ...
end
always # (CLOCK_PERIOD/2.0) clk = ~clk;

always @ (negedge clk)
begin
    #1
    begin
        if (in_read_cnt < 1)
            fir_val = 1'b0;
        else
            begin
                in_read_cnt = $fscanf(finput, "%d %d\n", fir_in, fir_val);

                if (in_read_cnt < 1)
                    begin
                        $fclose(finput);
                        fir_val = 1'b0;
                    end
                else
                    begin
                        end
                    end
            end
        end
    end
end
```

系统结构

萌